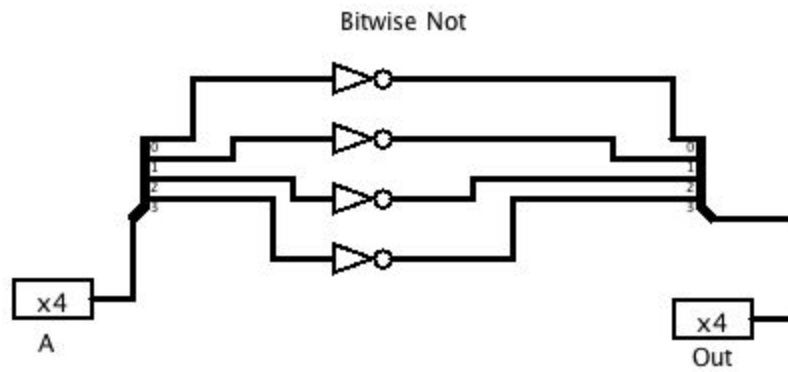


William "Chris" Fenton  
Mac, Rheanna, Naomi

### Lab1 - Bitwise Not Circuit



This circuit takes a 4-bit input and performs the negation operation on each pin.